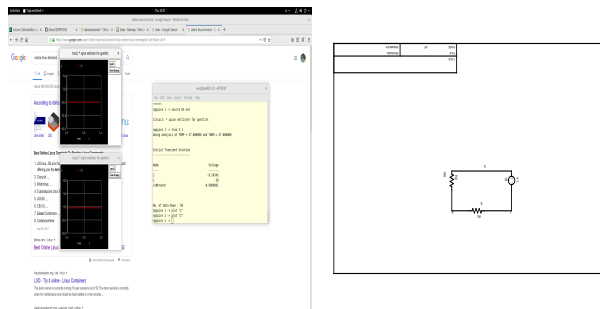


# laboratorywork2

dhruvsavani510

March 2020

## 1 Introduction



```
* spice netlist for gnetlist
V1 0 1 10
R2 0 1 105
R1 1 1 5
.END
```

in this project i make circuit with v1,r1,r2 and there's two nodes by using gschem and run circuit in ngspice.

I lear how to plot circuit in ngspice using gschem and add all details to LaTeX.  
THANK YOU!